

# HOMEWORK # 3 - March 17, 2020


## Part 1

Demonstrate the results shown in slides # 43-45 of the lecture "Analysis of unbalanced systems : the symmetrical components".

group	fault	slide #
MaEM	single line to ground	43
MaEL	double line to ground	45
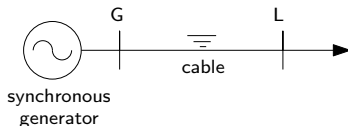
## Part 2

Consider the system shown below. A solid fault of the type specified in the above table takes place at bus L.



Using the technique described in the above slides compute :

- the voltage (in kV) between each phase and the ground at bus L
- the current (in A) in each phase of the cable
- the current in the fault (resp. each fault)

Generator :

- 5 MVA, 6 kV, connected in star, neutral grounded through a resistance of  $1 \Omega$
- $R_+ \simeq 0$ ,  $X_+ = X'' = 0.15$  pu
- $R_- = 0.01$  pu,  $X_- = 0.15$  pu
- $R_o \simeq 0$ ,  $X_o = 0.04$  pu

Cable :

- 6 kV, three-phase, single core with grounded shield
- $R_+ = 0.9 \Omega$ ,  $X_+ = 1.5 \Omega$ , shunt susceptance neglected
- $R_o = 4 \Omega$ ,  $X_o = 3 \Omega$ , shunt susceptance neglected

Load : connected in triangle

Operating point :

- (three-phase) power consumed by load : 2 MW / 0.8 Mvar
- voltage at bus L : 6 kV

*Make all calculations in per unit on the base :*

*single-phase power : 1 MVA      phase-to-neutral voltage :  $6/\sqrt{3}$  kV*

*E-mail your report to [t.vancutsem@uliege.be](mailto:t.vancutsem@uliege.be) no later than Sat March 28.*

*You will present it on March 31st (dedicated course)*